

Name: Ezgi

Surname: Demir

ID: 22103304

## EEE102 TERM PROJECT

### **Purpose:**

The objective of this project is to create a mini-basketball game using the BASYS3 development board. The game will utilize an IR (infrared) sensor to detect successful shots, and the points scored will be displayed on BASYS3's seven-segment display.

### **Design Specification:**

Here are the inputs and the outputs of my top-module. Also, you can see my modules in Figure 2.

#### **1. Inputs:**

- clk (std\_logic): Clock signal used for synchronization.
- reset (std\_logic): Reset signal for initializing the system.
- IR (std\_logic): Input signal from the IR sensor indicating the detection of a successful shot.

#### **2. Outputs:**

- sev\_seg (std\_logic\_vector(6 downto 0)): Output signal for displaying the score on the seven-segment display.
- anode\_sel (std\_logic\_vector(3 downto 0)): Output signal for selecting the active digit on the seven-segment display.

Also, as a sub-module I used a clock divider, The clock division is achieved using a counter mechanism. When the reset signal is high, the match1 signal and the count\_sig counter are both resets to their initial values. During the positive edge of the clk\_in signal, the counter is incremented. If the counter reaches the specified value, the match1 signal is updated according to a case statement. The counter is then reset to 0. This creates a divided clock signal with a frequency that is a fraction of the input clock frequency. In the basketball game project, I utilized a clock divider to manage the timing and synchronization of game components. By dividing the input clock frequency, a lower frequency clock signal was generated. This enabled precise coordination of the scoring mechanism, display updates, and IR sensor input processing. The clock divider ensured seamless operations, accurate point counting, and timely display updates. Its role in generating a slower clock signal facilitated smooth and synchronized gameplay.

Furthermore, In the seven\_segment sub-module, I worked with hexadecimal numbers to show them on my BASYS display.

### **Methodology:**

1. First, I have written my top-module main.vhd , inputs and outputs.
2. Then, I worked on my clkdivider.vhd sub-module.
3. After that, I began writing a code for the ultrasonic sensor without specifying which specific sensor I would use in my project. However, I encountered difficulties when trying to convert my distance display code into a score counter. Additionally, I faced issues with the trig and echo input and output. Consequently, I decided to change the sensor to the IR sensor (Figure 6), which would be more suitable for writing the code and integrating it into my basketball score-counting algorithm.
4. Then, the seven\_segment sub-module was written and all of these modules and other sub-modules were also brought together.
5. Finally, I ran my code, programmed my board, and made sensor connections with jumpers and breadboard. I used a sponge ball in order not to damage my sensor and also the hoop. Once I threw the ball through the basketball hoop the sensor which is connected to the breadboard under the hoop detects the balls. I adjusted my sensor the way that it detects objects under 5cm, I have adjusted this value considering the diameter of my hoop, therefore, it won't see any objects passing near the hoop or see me. I also control, if my reset button works properly (Figure 1 and 5). It resets the scoreboard on the seven-segment display hence, players can start again for example after the time runs out and compete with each other. That's why the reset button is crucial.
6. In my proposal I mentioned I could improve my project if I had adequate time however, I had a problem with the sensors and it took my time very much. Moreover, I couldn't move further since I have written I could maybe try the further steps in my proposal.

 


Figure 1: Reset button selected

## Results:

 


Figure 2: Elaborated Design of the code

 


Figure 3: Ball, before passing the hoop



 


Figure 4: Ball, after passing the hoop

 

*Figure 5: After pushing the “reset” button*

 

*Figure 6: IR sensor*

## **Conclusion:**

In conclusion, this project aimed to develop a mini-basketball game using the BASYS3 development board and an IR sensor for shot detection. The integration of modules such as the clock divider ensured precise timing and synchronization for smooth gameplay. Despite initial challenges with the ultrasonic sensor, the switch to the IR sensor enabled the successful implementation of the score-counting algorithm. While time constraints limited further improvements, the project demonstrated the functionality of the game and showcased the potential for future enhancements. Overall, the project successfully showcased the integration of hardware components and coding to create an engaging mini-basketball game.

**Youtube video link:**

<https://www.youtube.com/watch?v=HXj6WfAwCEI>

**References:**

- <https://how2electronics.com/bidirectional-visitor-counter-with-automatic-light-control-using-arduino/>
- EEE102 2023 Spring Semester Lecture Notes by Volkan Kurşun
- <https://www.realdigital.org/doc/9c21eab4a0f85c50486858a87380d1f6>

## **Appendices:**

### **main.vhd**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity Top is

Port (clk : in std\_logic;

reset : in std\_logic;

IR : in std\_logic;

sev\_seg : out std\_logic\_vector (6 downto 0);

anode\_sel : out std\_logic\_vector (3 downto 0));

end Top;

architecture Behavioral of Top is

component IR\_top

Port (clk : in std\_logic;

reset : in std\_logic;

IR : in std\_logic;

counterout : out std\_logic\_vector(15 downto 0));

end component;

component main\_sev\_seg

Port ( Counter\_out : in STD\_LOGIC\_VECTOR (15 downto 0);

Clk\_In : in STD\_LOGIC;

Seven\_segments : out STD\_LOGIC\_VECTOR (6 downto 0);

anod\_sel : out STD\_LOGIC\_VECTOR (3 downto 0));

```
end component;
```

```
signal count_out : STD_LOGIC_VECTOR(15 downto 0);
```

```
begin
```

```
UUT1 : IR_top
```

```
    port map (clk => clk,  
              reset => reset,  
              IR => IR,  
              counterout => count_out);
```

```
UUT2 : main_sev_seg
```

```
    port map (Counter_out => count_out,  
              Clk_In => clk,  
              Seven_segments => sev_seg,  
              anod_sel => anode_sel);
```

```
end Behavioral;
```

### **IR.vhd**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use ieee.numeric_std.ALL;
```

```
entity IR_top is
```

```
Port (clk : in std_logic;
```

```

    reset : in std_logic;
    IR : in std_logic;
    counterout : out std_logic_vector(15 downto 0));
end IR_top;

```

architecture Behavioral of IR\_top is

component sensor\_debounce is

```

    Generic (
        clk_freq: integer := 100_000_000;
        debounce_freq: integer := 10000);
    Port (
        clk: in std_logic;
        sensor_in: in std_logic;
        sensor_out: out std_logic
    );
end component;

```

```

signal counter : integer := 0;
signal Debounce_IR: std_logic;
begin

```

```

Debounce: sensor_debounce generic map(debounce_freq => 100000)
port map( clk => clk, sensor_in => IR, sensor_out => Debounce_IR );

```

```

process(clk, reset)
    variable IR_prev : std_logic := '1'; -- Initialize previous IR value to '1'
begin

```



```

if reset = '1' then
    counter <= 0;
    IR_prev := '1'; -- Reset the previous IR value

elsif rising_edge(clk) then
    if Debounce_IR = '0' and IR_prev = '1' then
        counter <= counter + 1;
    end if;

    IR_prev := Debounce_IR; -- Store the current IR value for the next clock cycle
end if;
end process;

counterout <= std_logic_vector(to_unsigned(counter, 16));

end Behavioral;

```

### **clkdivider.vhd**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity point_clk_divider is
    Port ( clk_in : in STD_LOGIC;
          Reset : in STD_LOGIC;
          clk_out : out STD_LOGIC_VECTOR (1 downto 0));
end point_clk_divider;

architecture Behavioral of point_clk_divider is

```

```
SIGNAL match1 : STD_LOGIC_VECTOR (1 DOWNTO 0);
```

```
SIGNAL count_sig : INTEGER RANGE 0 TO 6249 :=0;
```

```
begin
```

```
PROCESS (Reset, clk_in)
```

```
BEGIN
```

```
IF( Reset = '1') THEN
```

```
    match1 <= "00";
```

```
    count_sig <= 0;
```

```
ELSIF RISING_EDGE(clk_in) THEN
```

```
    IF(count_sig = 6249) THEN
```

```
        CASE match1 IS
```

```
            WHEN "00" => match1 <= "01";
```

```
            WHEN "01" => match1 <= "10";
```

```
            WHEN "10" => match1 <= "11";
```

```
            WHEN others => match1 <= "00";
```

```
        END CASE;
```

```
        count_sig <= 0;
```

```
    ELSE
```

```
        count_sig <= count_sig + 1;
```

```
    END IF;
```

```
END IF;
```

```
END PROCESS;
```

```
clk_out <= match1;
```

```
end Behavioral;
```

### **seven.seg.vhd**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

use IEEE.NUMERIC\_STD.ALL;

use IEEE.STD\_LOGIC\_UNSIGNED.ALL;

entity main\_sev\_seg is

Port ( Counter\_out : in STD\_LOGIC\_VECTOR (15 downto 0);

Clk\_In : in STD\_LOGIC;

Seven\_segments : out STD\_LOGIC\_VECTOR (6 downto 0);

anod\_sel : out STD\_LOGIC\_VECTOR (3 downto 0));

end main\_sev\_seg;

architecture Behavioral of main\_sev\_seg is

COMPONENT multiplexer

PORT ( Counter\_out : in STD\_LOGIC\_VECTOR (15 downto 0);

sev\_sel : in STD\_LOGIC\_VECTOR (1 downto 0);

mux\_out : out STD\_LOGIC\_VECTOR (3 downto 0));

END COMPONENT;

COMPONENT seven\_segment

PORT ( out\_of\_mux : in STD\_LOGIC\_VECTOR (3 downto 0);

seven\_seg : out STD\_LOGIC\_VECTOR (6 downto 0));

END COMPONENT;

COMPONENT point\_clk\_divider

PORT ( clk\_in : in STD\_LOGIC;

Reset : in STD\_LOGIC;

```
clk_out : out STD_LOGIC_VECTOR (1 downto 0));
```

```
END COMPONENT;
```

```
COMPONENT inv_decoder
```

```
PORT ( input : in STD_LOGIC_VECTOR (1 downto 0);
```

```
output : out STD_LOGIC_VECTOR (3 downto 0));
```

```
END COMPONENT;
```

```
SIGNAL temp_dig : STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
SIGNAL temp_reset : STD_LOGIC;
```

```
SIGNAL temp_clk : STD_LOGIC_VECTOR (1 DOWNTO 0);
```

```
begin
```

```
OPP1 : multiplexer
```

```
PORT MAP (Counter_out => Counter_out,
```

```
sev_sel (1 DOWNTO 0) => temp_clk (1 DOWNTO 0),
```

```
mux_out (3 DOWNTO 0) => temp_dig (3 DOWNTO 0));
```

```
OPP2 : seven_segment
```

```
PORT MAP (out_of_mux (3 DOWNTO 0) => temp_dig (3 DOWNTO 0),
```

```
seven_seg (6 DOWNTO 0) => Seven_segments (6 DOWNTO 0));
```

```
OPP3 : point_clk_divider
```

```
PORT MAP (clk_in => Clk_In,
```

```
Reset => temp_reset,
```

```
clk_out (1 DOWNTO 0) => temp_clk (1 DOWNTO 0));
```

```
OPP4 : inv_decoder
```

```
PORT MAP (input (1 DOWNT0 0) => temp_clk (1 DOWNT0 0),  
output (3 DOWNT0 0) => anod_sel (3 DOWNT0 0));
```

```
end Behavioral;
```

### **seven\_segment.vhd**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity seven_segment is
```

```
Port ( out_of_mux : in STD_LOGIC_VECTOR (3 downto 0);
```

```
      seven_seg : out STD_LOGIC_VECTOR (6 downto 0));
```

```
end seven_segment;
```

```
architecture Behavioral of seven_segment is
```

```
begin
```

```
PROCESS(out_of_mux)
```

```
BEGIN
```

```
CASE out_of_mux IS
```

```
WHEN "0000" => seven_seg <= "1000000"; -- 0
```

```
WHEN "0001" => seven_seg <= "1111001"; -- 1
```

```
WHEN "0010" => seven_seg <= "0100100"; -- 2
```

```
WHEN "0011" => seven_seg <= "0110000"; -- 3
```

```
WHEN "0100" => seven_seg <= "0011001"; -- 4
```

```
WHEN "0101" => seven_seg <= "0010010"; -- 5
```

```

WHEN "0110" => seven_seg <= "0000010"; -- 6
WHEN "0111" => seven_seg <= "1111000"; -- 7
WHEN "1000" => seven_seg <= "0000000"; -- 8
WHEN "1001" => seven_seg <= "0011000"; -- 9
WHEN "1010" => seven_seg <= "0001000"; -- 10 -> A
WHEN "1011" => seven_seg <= "0000011"; -- 11 -> b
WHEN "1100" => seven_seg <= "1000110"; -- 12 -> C
WHEN "1101" => seven_seg <= "0100001"; -- 13 -> d
WHEN "1110" => seven_seg <= "0000110"; -- 14 -> E
WHEN others => seven_seg <= "0001110"; -- 15 -> F
END CASE;
END PROCESS;

```

end Behavioral;

### **return.vhd**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity sensor_debounce is
    Generic (
        clk_freq: integer := 100_000_000;
        debounce_freq: integer := 10000);
    Port (
        clk: in std_logic;
        sensor_in: in std_logic;
        sensor_out: out std_logic
    );
end sensor_debounce;

```

architecture Behavioral of sensor\_debounce is

constant timer\_limit: integer := clk\_freq/debounce\_freq;

type debounce\_state is (ZERO, RISE, ONE, FALL);

signal state: debounce\_state := ZERO;

signal timer\_enable: std\_logic := '0';

signal timer\_out: std\_logic := '0';

signal timer: integer range 0 to timer\_limit := 0;

begin

StateMachine: process(clk) begin

if rising\_edge(clk) then

case state is

when ZERO =>

sensor\_out <= '0';

if sensor\_in = '1' then

state <= RISE;

end if;

when RISE =>

sensor\_out <= '0';

timer\_enable <= '1';

if timer\_out = '1' then

state <= ONE;

timer\_enable <= '0';

end if;

if sensor\_in = '0' then

state <= ZERO;

```

        timer_enable <= '0';
    end if;
when ONE =>
    sensor_out <= '1';
    if sensor_in = '0' then
        state <= FALL;
    end if;
when FALL =>
    timer_enable <= '1';
    sensor_out <= '1';
    if timer_out = '1' then
        state <= ZERO;
        timer_enable <= '0';
    end if;
    if sensor_in = '1' then
        state <= ONE;
        timer_enable <= '0';
    end if;
end case;
end if;
end process;

```

```

TimerProcesss: process(clk) begin
    if rising_edge(clk) then
        if timer_enable = '1' then
            if (timer = timer_limit - 1) then
                timer_out <= '1';
                timer <= 0;
            else

```



```

        timer <= timer + 1;

        timer_out <= '0';
    end if;

else

    timer <= 0;

    timer_out <= '0';

end if;

end if;

end process;

```

end Behavioral;

#### **mux.vhd**

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity multiplexer is
    Port ( Counter_out : in STD_LOGIC_VECTOR (15 downto 0);
-- grp1 : in STD_LOGIC_VECTOR (3 downto 0);
-- grp2 : in STD_LOGIC_VECTOR (3 downto 0);
-- grp3 : in STD_LOGIC_VECTOR (3 downto 0);
-- grp4 : in STD_LOGIC_VECTOR (3 downto 0);
    sev_sel : in STD_LOGIC_VECTOR (1 downto 0);
    mux_out : out STD_LOGIC_VECTOR (3 downto 0));
end multiplexer;

```

architecture Behavioral of multiplexer is

```
SIGNAL match : STD_LOGIC_VECTOR (3 DOWNTO 0);
```

```
begin
```

```
PROCESS (Counter_out, sev_sel)
```

```
BEGIN
```

```
CASE sev_sel IS
```

```
WHEN "00" => match <= Counter_out(3 downto 0);
```

```
WHEN "01" => match <= Counter_out(7 downto 4);
```

```
WHEN "10" => match <= Counter_out(11 downto 8);
```

```
WHEN others => match <= Counter_out(15 downto 12);
```

```
END CASE;
```

```
mux_out <= match;
```

```
END PROCESS;
```

```
end Behavioral;
```

### **invertdecoder.vhd**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity inv_decoder is
```

```
Port ( input : in STD_LOGIC_VECTOR (1 downto 0);
```

```
output : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end inv_decoder;
```

```
architecture Behavioral of inv_decoder is
```

```
begin
```

```
PROCESS(input)
BEGIN
CASE input IS
  WHEN "00" => output <= "1110";
  WHEN "01" => output <= "1101";
  WHEN "10" => output <= "1011";
  WHEN "11" => output <= "0111";
  WHEN others => output <= "0000";
END CASE;
END PROCESS;
end Behavioral;
```